
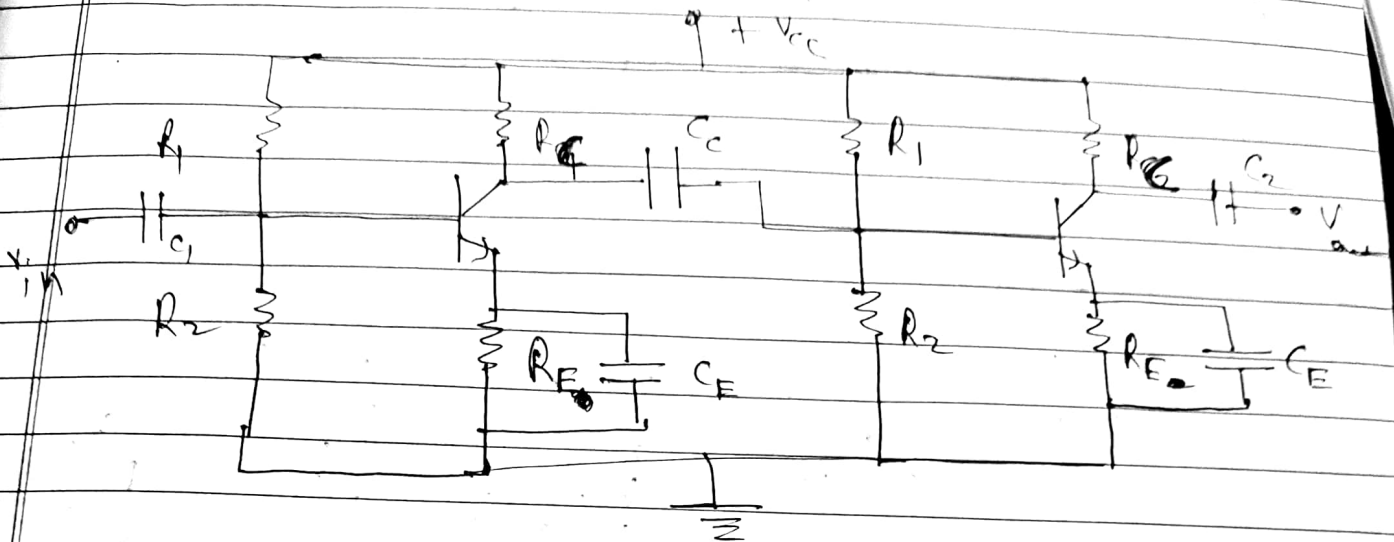


RC Coupled Amplifiers

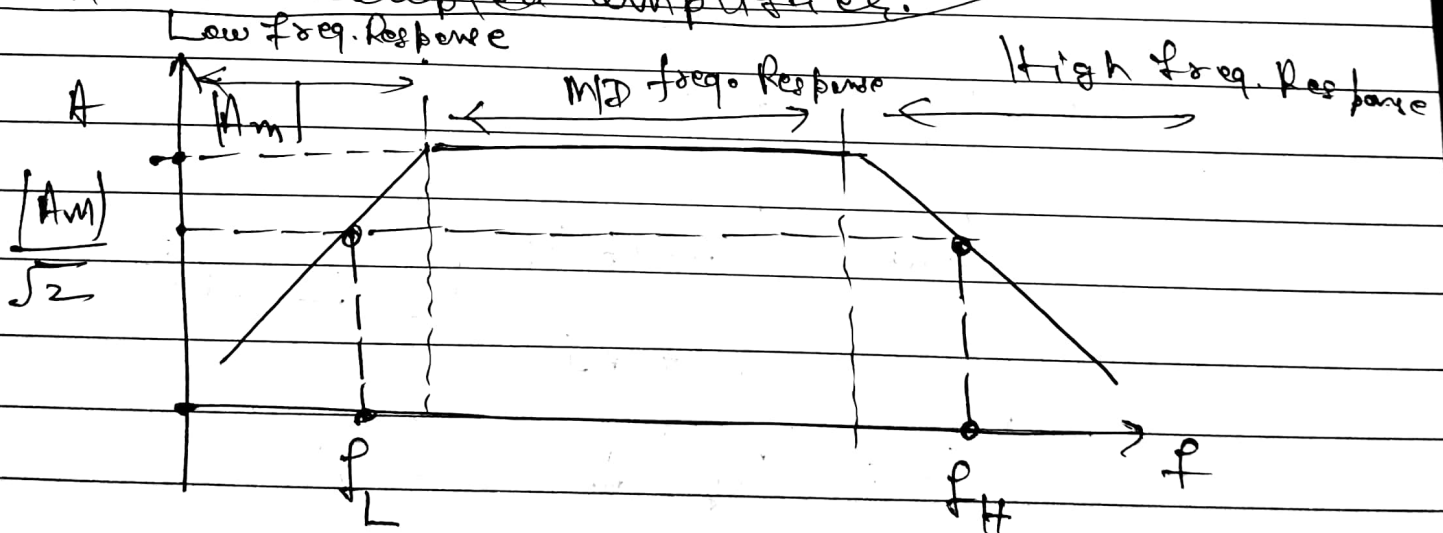

It consists of the two potential divider common emitter amplifier circuits as shown. The output of 1 produces β given to the other through the coupling capacitor (C_c). Following is the frequency response of the RC coupled amplifiers.




Bandwidth

$$= (f_H - f_L)$$

A = gain (Voltage) $\frac{V_s}{V_i}$ Frequency graph.

Case 1

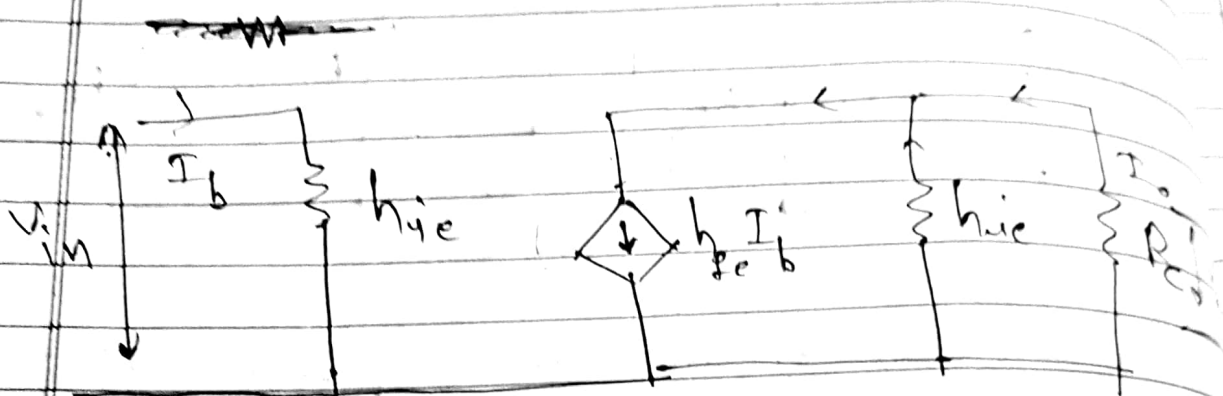mid frequency analysis of the RC coupled amplifier



By current divider Rule

$$I_o = \frac{h_{ie}}{R_c + h_{ie}} \times h_{fe} I_b$$

$$V_{out} = I_o R_c$$

$$V_{out} = \frac{h_{ie} h_{fe} I_b R_c}{R_c + h_{ie}} \quad \text{--- (1)}$$


$$V_{in} = I_b h_{ie} \quad \text{--- (2)}$$

Dividing (1) by (2)


$$\frac{V_{out}}{V_{in}} = \frac{\cancel{h_{ie}} h_{fe} I_b R_c}{R_c + h_{ie} \cancel{I_b / h_{ie}}}$$

$$\Rightarrow A_{v_m} = \frac{h_{fe} R_c}{R_c + h_{ie}}$$

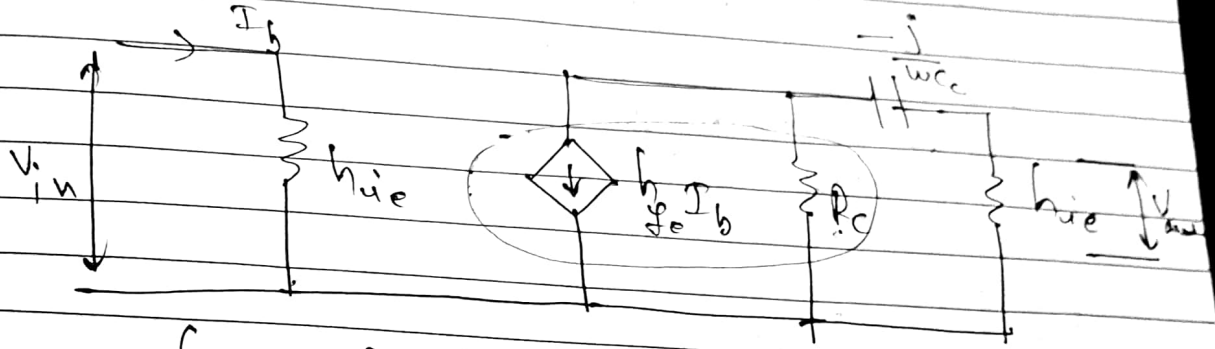Case-2 Low frequency analysis of RC-coupled amplifiers. We ~~can~~ ^{now} consider the capacitor in the circuit.



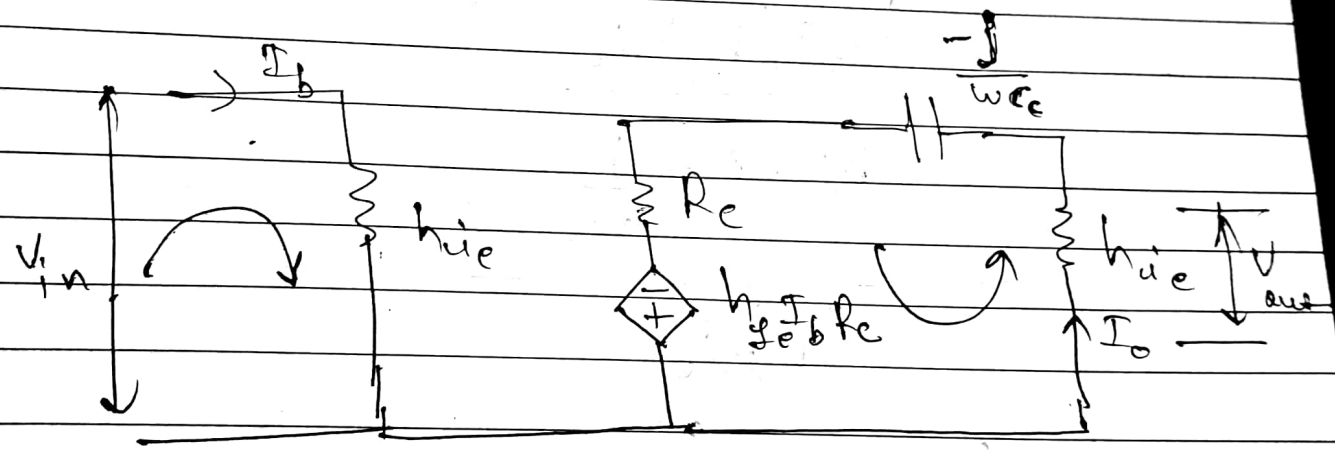Converting current source into voltage source



$$V_{in} = I_b h_{ie} \quad \text{--- (1)}$$

$$h_{fe} I_b R_c = I_o h_{ie} - \frac{j}{\omega C_c} I_o + R_c I_o$$

$$I_o = \frac{h_{fe} I_b R_c}{(h_{ie} + R_c - \frac{j}{\omega C_c})}$$

$$V_{out} = I_{out} h_{ie}$$

$$V_{out} = \frac{h_{fe} I_b R_c h_{ie}}{h_{ie} + R_c - \frac{j}{\omega C}}$$

Low frequency
Voltage gain

$$A_{v_e} = \frac{V_{out}}{V_{in}}$$

$$A_{v_e} = \frac{h_{fe} I_b R_c h_{ie}}{h_{ie} + R_c - \frac{j}{\omega C}}$$

$$\cancel{I_b h_{ie}}$$

$$A_{v_e} = \frac{(h_{fe} R_c)}{(h_{ie} + R_c - \frac{j}{\omega C})}$$

$$\frac{(h_{fe} R_c)}{(h_{ie} + R_c - \frac{j}{\omega C})}$$

Dividing Num. &

Den. by $(h_{ie} + R_c)$

$$A_{v_e} = \frac{\left(\frac{h_{se} R_c}{h_{ie} + R_c} \right)}{1 - j \omega_c (h_{ie} + R_c)}$$

$$A_{v_e} = \frac{A_{v_m}}{1 - j \omega_c (h_{ie} + R_c)}$$


Taking its modulus we get

$$|A_{v_e}| = \frac{|A_{v_m}|}{\sqrt{1 + \frac{1}{(\omega_c (h_{ie} + R_c))^2}}}$$


Cutoff frequency is

$$f_c = \frac{1}{2\pi C (h_{ie} + R_c)}$$

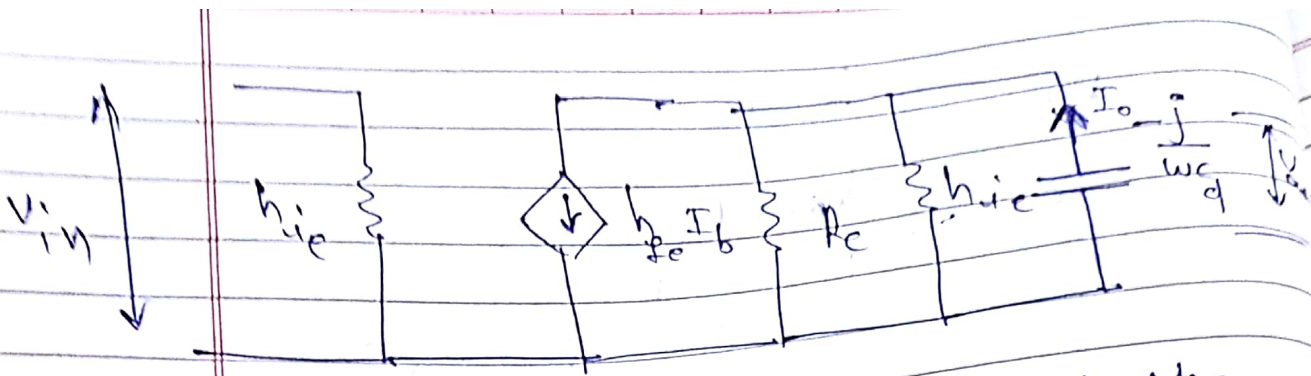Case-3 High frequency analysis of the amplifier



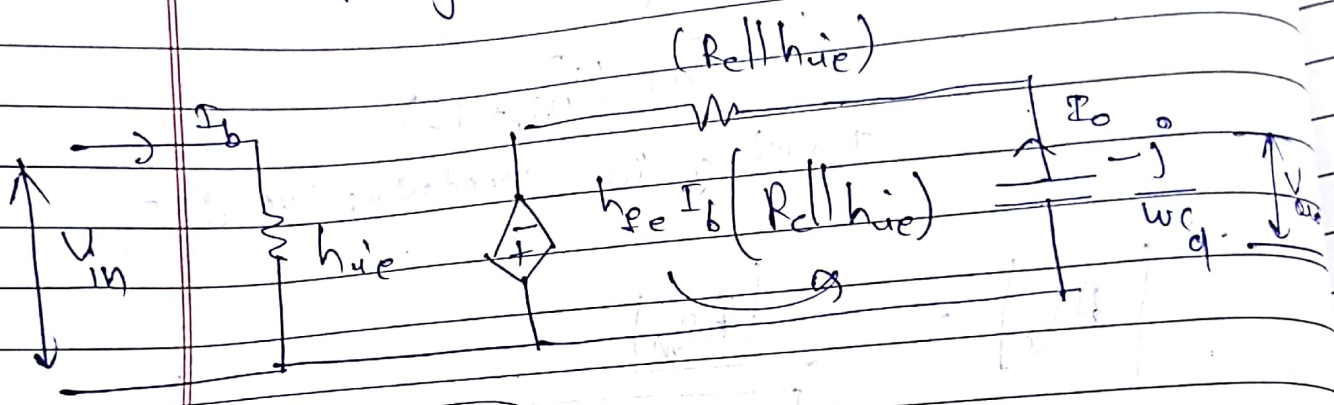Let $C_d =$ Diffusion capacitance of the transistor pn -junction



$V_{in} = I_b h_{ie}$ — (1)
K.V.L in the output loop

$$h_{fe} I_b (R_c || h_{ie}) = \frac{-j}{\omega C_d} I_o + (R_c || h_{ie}) I_o$$

$$I_o = \frac{h_{fe} I_b (R_c || h_{ie})}{(R_c || h_{ie}) - \frac{j}{\omega C_d}}$$

$$(R_c || h_{ie}) - \frac{j}{\omega C_d}$$

$$V_{out} = I_o \left[\frac{j}{\omega C_d} \right]$$

$$V_{out} = \frac{h_{fe} I_b (R_c || h_{ie})}{(R_c || h_{ie}) - \frac{j}{\omega C_d}} - \left(\frac{-j}{\omega C_d} \right)$$

$$V_{out} = \frac{h_{fe} I_b (R_c || h_{ie})}{\left(\frac{(R_c || h_{ie})}{(-j/\omega C_d) + 1} \right)}$$

$$V_{out} = \frac{h_{fe} I_b (R_c || h_{ie})}{\left(\frac{j R_c || h_{ie} \omega C_d + 1}{(R_c + h_{ie})} \right)}$$

$$V_{out} = V_{in} \left(\frac{h_{fe} R_c}{R_c + h_{ie}} \right)$$

$$1 + j (R_c || h_{ie}) \omega C_d$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{A_{vm}}{1 + j (\omega C_d) (R_c || h_{ie})}$$


$$|A_v| = \frac{|A_{vm}|}{\sqrt{1 + (\omega C_d (R_c || h_{ie}))^2}}$$

Upper Cutoff freq.

~~$f_H = \frac{1}{2\pi(R_c || h_{ie})C_d}$~~

$$f_H = \frac{1}{2\pi(R_c || h_{ie})C_d}$$

CASCADED AMPLIFIER

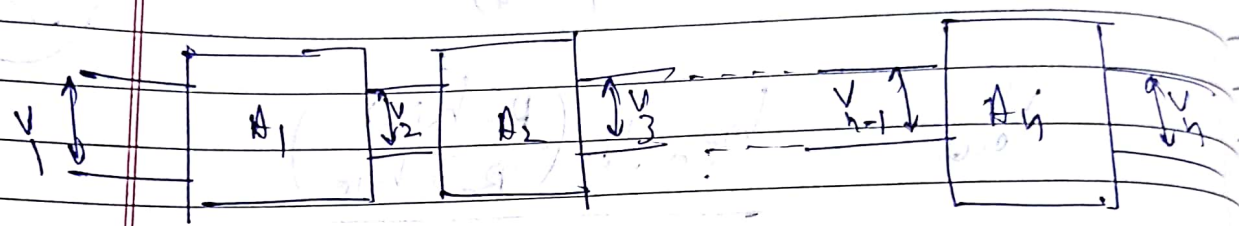

$$A_1 = \frac{V_2}{V_1} \quad \text{--- (1)}$$

$$A_2 = \frac{V_3}{V_2} \quad \text{--- (2)}$$

$$A_n = \frac{V_n}{V_{n-1}} \quad \text{--- (n)}$$

Multiplying

$$(1) \times (2) \dots \times (n)$$

$$A_1 A_2 \dots A_n = \frac{V_2}{V_1} \times \frac{V_3}{V_2} \times \frac{V_4}{V_3} \times \dots \times \frac{V_n}{V_{n-1}}$$

$$A_1 A_2 \dots A_n = \frac{V_n}{V_1} = A \text{ (overall gain)}$$

$$\therefore A = A_1 A_2 A_3 \dots A_n$$

CASCADE AMPLIFIER

If we connect common emitter amplifiers in cascade with the common base amplifier, then it is known as cascade amplifier.

